Name: - Himanshu Rathod

ID NO.: - 19EL063

Division: - 04

Year: - 2023-24

Subject: - Digital System Design (3EL42)

Branch: - Electronics (EL)


Q1. CLOCK DIVIDER

VERILOG CODE: -

```
module Clock_divider(
    input clock_in,
    output reg clock_out
    );
reg[27:0] counter=28'd0;
parameter DIVISOR = 28'd2;
always @(posedge clock_in)
begin
    counter <= counter + 28'd1;
if(counter>=(DIVISOR-1))
    counter <= 28'd0;
    clock_out <= (counter<DIVISOR/2)?1'b1:1'b0;
end
endmodule</pre>
```

TEST BENCH: -
 
```
module tb_clock_divider;
reg clock_in;
wire clock_out;
clock_divider uut (
    .clock_in(clock_in),
    .clock_out(clock_out)
);
initial begin
clock_in = 0;
    forever #10 clock_in = ~clock_in;
end
endmodule
```




SYNTHESIS REPORT: -

```
source clock divider.tcl -notrace
Command: synth_design -top clock_divider -part xc7k70tfbv676-1
Starting synth_design
Attempting to get a license for feature 'Synthesis' and/or device 'xc7k70t'
INFO: [Common 17-349] Got license for feature 'Synthesis' and/or device 'xc7k70t'
INFO: [Synth 8-7079] Multithreading enabled for synth_design using a maximum of 2 processes.
INFO: [Synth 8-7078] Launching helper process for spawning children vivado processes
INFO: [Synth 8-7075] Helper process launched with PID 11392
Starting Synthesize : Time (s): cpu = 00:00:04 ; elapsed = 00:00:07 . Memory (MB): peak = 1046.367 ; gain = 0.000
INFO: [Synth 8-6157] synthesizing module 'clock_divider' [E:/projects dsd/clock_divider 1/clock_divider 1.srcs/sources_1/nei
   INFO: [Synth 8-6155] done synthesizing module 'clock_divider' (1#1) [E:/projects dsd/clock_divider 1/clock_divider 1.srcs/se
Finished Synthesize : Time (s): cpu = 00:00:05 ; elapsed = 00:00:08 . Memory (MB): peak = 1046.367 ; gain = 0.000
Report BlackBoxes:
+-+----+
| |BlackBox name |Instances |
+-+----+
+-+----+
Report Cell Usage:
+----+
      |Cell |Count |
11
      BUFG
12
      CARRY4
                  71
13
      |LUT1 |
                  11
14
      LUT4
                  11
15
      LUT5
                  21
16
      LUT6
                  81
17
      FDRE
                 291
      LIBUF
```

```
13
      |LUT1 |
                  11
|4
     |LUT4 |
15
     |LUT5 |
                  21
16
      |LUT6
                  81
            1
17
      FDRE
                 291
18
     | IBUF
                 11
    |OBUF |
Report Instance Areas:
     |Instance |Module |Cells |
            | | 51|
11
    |top
Finished Writing Synthesis Report : Time (s): cpu = 00:00:15 ; elapsed = 00:00:29 . Memory (MB): peak = 1046.367 ; gain = 0
```

POWER REPORT: -

 

Q2. Johnson Counter

VERILOG CODE: -

```
`timescale lns / lps
module johnson_counter(
     input clk,
     input reset,
     output [3:0] out
     reg [3:0] q;
always @(posedge clk)
begin
if(reset)
  q=4'd0;
  else
   begin
     q[3]<=q[2];
       q[2]<=q[1];
  a[1]<=a[0]:
always @(posedge clk)
begin
if (reset)
  q=4'd0;
   else
     begin
          q[3]<=q[2];
          q[2]<=q[1];
          q[1]<=q[0];
          q[0] <= (\sim q[3]);
    end
end
  assign out=q;
) endmodule
```

TEST BENCH: -

```
"timescale lns / lps

module jc_tb;
  reg clk,reset;
  wire [3:0] out;

johnson_counter dut (.out(out), .reset(reset), .clk(clk));

always
  #5 clk =~clk;

initial begin
  reset=l'bl; clk=l'b0;
  #20 reset= l'b0;
end

initial
  begin
```


```
johnson_counter dut (.out(out), .reset(reset), .clk(clk));

always
    #5 clk =~clk;


initial begin
    reset=1'b1; clk=1'b0;
#20 reset= 1'b0;
end

initial
    begin
    $monitor($time, " clk=8b, out= %b, reset=8b", clk,out,reset);
    #105 $stop;
end


endmodule
```

 

SYNTHESIS REPORT: -

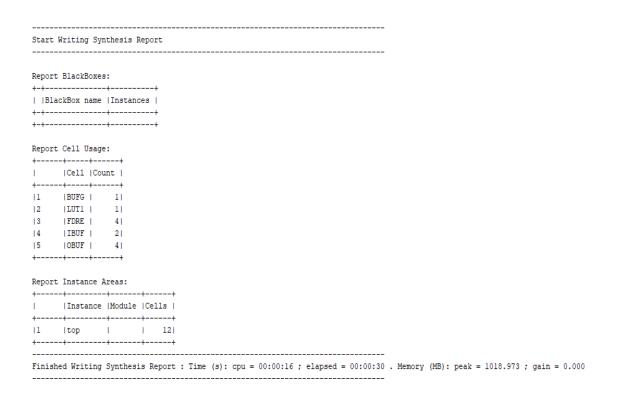

POWER REPORT: -

 


Q3. RING COUNTER

VERILOG CODE: -


```
ring_counter.v
                                                                                             ? 🗆 🖒 X
E:/projects dsd/RING COUNTER/ring counter.srcs/sources_1/new/ring_counter.v
Q | 🛗 | ♠ | → | 🐰 | 🖺 | 🖍 | // | 🖩 | ♀
                                                                                                     Ö
1 ;
2 =
         'timescale lns / lps
         module ring_counter(
           input Clock,
3
           input Reset,
5
           output [3:0] Count_out
           );
6
7
           reg [3:0] Count_temp;
always @(posedge(Clock),Reset)
8 🖨
9 🖯
           begin
10 🛱
               if(Reset == 1'bl) begin
11 🔅
                    Count_temp = 4'b0001;
12 🗦
               else if(Clock == 1'bl) begin
13
14 🗀
                    Count_temp = {Count_temp[2:0],Count_temp[3]}; end
15 🖨
           end
16
            assign Count_out = Count_temp;
17 🖨
         endmodule
18
```

TEST BENCH: -
 
```
module tb ring;
   reg Clock;
    reg Reset;
    wire [3:0] Count out;
    ring_counter uut (
        .Clock(Clock),
        .Reset (Reset),
        .Count_out (Count_out)
    );
    initial Clock = 0;
    always #10 Clock = ~Clock;
    initial begin
        Reset = 1;
        #50;
        Reset = 0;
    end
endmodule
```



SYNTHESIS REPORT: -

 

POWER REPORT: -

Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

1.069 W Total On-Chip Power:

Design Power Budget: Not Specified

Power Budget Margin: N/A Junction Temperature: 27.0°C


Thermal Margin: 58.0°C (30.6 W)

Effective 9JA: 1.9°C/W

Power supplied to off-chip devices: 0 W Confidence level:

Launch Power Constraint Advisor to find and fix

invalid switching activity

 


Q4. 5 INPUT MAJORITY CIRCUIT

VERILOG CODE: -

```
module majority_of_five(
    input [4:0] sw,
    output led
    );
assign led = (sw[0] & sw[1] & sw[2]) |
        (sw[0] & sw[1] & sw[3]) |
        (sw[0] & sw[1] & sw[4]) |
        (sw[0] & sw[2] & sw[3]) |
        (sw[0] & sw[2] & sw[4]) |
        (sw[0] & sw[3] & sw[4]) |
        (sw[1] & sw[2] & sw[4]) |
        (sw[1] & sw[2] & sw[4]) |
        (sw[1] & sw[3] & sw[4]) |
        (sw[1] & sw[3] & sw[4]) |
        (sw[1] & sw[3] & sw[4]) |
        (sw[2] & sw[3] & sw[4]);
endmodule
```

TEST BENCH:-
 
```
module majority_of_five_tb;
     reg [4:0] sw;
      wire led;
      majority_of_five cut (.sw(sw),.led(led));
      integer k;
     initial
Э
     begin
         sw = 0;
         for (k=0; k<32; k=k+1)
Э
             #20 sw = k;
É
         #20 $finish;
É
      end
      endmodule
```



SYNTHESIS REPORT:-

	Writing Syn		-																			
+-+	BlackBoxes	+																				
+ + 1 2 3 +	Cell Usage	nt nt + 1 5 1 +																				
Ī	Instance	Module	Cells																			
1 +	-+ top -+	+	7 +																			
Finish	ed Writing	Synthesi	s Report	: Time	(s):	cpu =	= 00:0	0:16	; elap	sed =	00:00	0:27	. Men	nory	(MB):	peak	= 10	18.27	13 ;	gain	= 0	.000

POWER REPORT:-

Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.478 W

Design Power Budget: **Not Specified**


Power Budget Margin: N/A 25.9°C **Junction Temperature:**

Thermal Margin: 59.1°C (31.2 W)

Effective 9JA: 1.9°C/W Power supplied to off-chip devices: 0 W

Confidence level:
 
<u>Launch Power Constraint Advisor</u> to find and fix invalid switching activity



Q5.PARITY GENERATOR

VERILOG CODE:-

```
parity_generator.v
                                                                             ? 🗆 🖰 X
E:/projects dsd/PARITY GENERATOR/PARITY GENERATOR.srcs/sources_1/new/parity_generator.v
                                                                                    Х
٥
       // Additional Comments:
18
19 ;
20 🖨
21
22
23 🖨
      module parity(
24
          input x,
25
          input y,
26
         input z,
27
         output result
28
          );
29 xor (result, x, y, z);
30
31 🖯
        endmodule
32
```

TEST BENCH:-

```
bodule parity_tb
fsg.Ky.V.Si
Minitial begin
x = 0;
y = 0;
t = 0;

$100;
x = 0;
y = 0;
t = 1;

$100;
x = 0;
y = 1;
t = 0;
$100;
x = 0;
y = 1;
t = 0;
$100;
x = 0;
y = 1;
t = 0;
$100;
x = 0;
y = 1;
t = 1;
$100;
x = 0;
y = 1;
t = 1;
$100;
x = 0;
y = 1;
t = 1;
$100;
x = 0;
y = 1;
t = 1;
$100;
x = 0;
y = 1;
t = 0;
y = 0;
t = 0;
t
```

```
#100;

x = 1;

y = 0;

z = 1;

#100;

x = 1;

y = 1;

z = 0;

#100;


x = 1;

y = 1;

z = 1;

y = 1;

z = 1;
```

 

SYNTHESIS REPORT:-

Start Writing Synthesis Report

Report BlackBoxes:								
+-+		+						
BlackBox	name	Instances						
+-+		+						

+-+----

		Count
,	T	
11	LUT3	1
12	IBUF	3
13	OBUF	1 11
4		

Report Instance Areas:

+	+	+	++
i	Instance		
1	top	I	51
+	+	+	++

Finished Writing Synthesis Report : Time (s): cpu = 00:00:16 ; elapsed = 00:13:45 . Memory (MB): peak = 1014.574 ; gain = 0.000

POWER REPORT:-

Summary



Total On-Chip Power: 0.661 W

Design Power Budget: Not Specified


N/A

Junction Temperature:26.2°CThermal Margin:58.8°C (31.0 W)Effective θJA:1.9°C/WPower supplied to off-chip devices:0 WConfidence level:Low

<u>Launch Power Constraint Advisor</u> to find and fix

invalid switching activity

Power Budget Margin:

 


Q6. BINARY TO ONE HOT ENCODER

VERILOG CODE:-


```
module decoder_3_8(a, b, c, out);
  input a,b,c;
  output [7:0] out;
  assign out [0] = (~as~bs~c);
  assign out [1] = (~as~bs~c);
  assign out [2] = (~asbs~c);
  assign out [3] = (~asbs~c);
  assign out [4] = (as~bs~c);
  assign out [5] = (as~bs~c);
  assign out [6] = (asbs~c);
  assign out [7] = (asbs~c);
```

TEST BENCH:-
 
```
module test_decoder;
reg a, b,c;
wire [7:0] out;
decoder_3_8 DUT(a,b,c,out);
initial
begin
$monitor($time, "a=%b , b=%b , c=%b , out = %b" , a,b,c,out);
a=0 ; b=0 ;c=0 ;
# 100
a=0 ; b=0 ;c=1 ;
#100
a=0 ; b=1 ;c=0 ;
#100
a=1 ; b=1 ;c=1 ;
#100 $finish;
end
endmodule
```



SYNTHESIS REPORT:-

 

POWER REPORT:-

Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 1.393 W
Design Power Budget: Not Specified

Power Budget Margin: N/A

Junction Temperature: 27.6°C
Thermal Margin: 57.4°C (30.3 W)


Effective &JA: 1.9°C/W

Power supplied to off-chip devices: 0 W

Confidence level: Low

Launch Power Constraint Advisor to find and fix

invalid switching activity

 

Q7. 4-BIT BCD SYNCHRONOUS COUNTER


VERILOG CODE:-

```
Project Summary × 4b_syn_counter.v ×
                                                                                                                ? 🗗
E:/projects dsd/4-BIT BCD SYNCHRONOUS COUNTER/4-BIT BCD SYNCHRONOUS COUNTER.srcs/sources_1/new/4b_syn_counter.v
15 //
16 // Revision:
17 // Revision 0.01 - File Created
18 // Additional Comments:
19 //
21 🖯 module bcd_counter(input clk, reset, output reg [3:0] q);
22 reg [3:0] t;
23 - always @ (posedge clk) begin
24 🖯 if (reset)
25 🖯 begin
     t <= 4'b0000;
26
27
      q <= 4'b0000;
28 🗀 end
29
     else
30 🖯 begin
      t <= t + 1;
31
32 🖯
      if (t == 4'b1001)
33 🔁 begin
34
       t <= 4'b0000;
35 ← end
36
      q <= t;
38 🖨 end
39 🗎 endmodule
```

TEST BENCH:-

```
41
42
43
44 \(\overline{\top}\) module bcd_counter_tb;
45 reg clk;
46 reg reset;
47 wire [3:0] q;
49 bcd_counter DUT(.clk(clk), .reset(reset), .q(q));
50 initial begin
    clk = 0;
forever #5 clk = ~clk;
51
52
53 🖨 end
54
55 o initial begin
        #10 reset = 0;

 $monitor ("T=80t out=8b", $time, q);
        #150 reset = 1;
59
      #10 reset = 0;
61
      #200
$finish;
64 endmodule
```



SYNTHESIS REPORT:-

```
Start Writing Synthesis Report
Report BlackBoxes:
| |BlackBox name |Instances |
+-+----
Report Cell Usage:
    |Cell |Count |
11
      |BUFG |
      |LUT1 |
12
                11
      |LUT3 |
13
      |LUT4 |
|5
|6
      |FDRE |
               81
      |IBUF |
               21
      |OBUF |
Report Instance Areas:
     |Instance |Module |Cells |
+----+
Finished Writing Synthesis Report : Time (s): cpu = 00:00:14 ; elapsed = 00:00:26 . Memory (MB): peak = 1018.500 ; gain = 0.000
```

POWER REPORT:-

Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 3.609 W

Design Power Budget: Not Specified


Power Budget Margin: N/A Junction Temperature: 31.8°C

Thermal Margin: 53.2°C (28.1 W)

Effective 9JA: 1.9°C/W

Power supplied to off-chip devices: 0 W Confidence level:
 
<u>Launch Power Constraint Advisor</u> to find and fix invalid switching activity




Q8. 4-BIT CARRY LOOKAHEAD ADDER

VERILOG CODE:-


```
| Mark |
```

TEST BENCH:-
 
```
module TestModule;
reg [3:0] a;
reg [3:0] b;
reg cin;
wire [3:0] sum;
wire cout;
CLA_Adder uut (
.a(a),
.b(b),
.cin(cin),
.sum(sum),
.cout (cout)
initial begin
a = 0;
b = 0;
cin = 0;
#100;
a = 5;
b = 6;
cin = 1;
#100;
end
endmodule
```



SYNTHESIS REPORT:-

 

Finished Writing Synthesis Report : Time (s): cpu = 00:00:18 ; elapsed = 00:00:32 . Memory (MB): peak = 1015.535 ; gain = 0.000

POWER REPORT:-

Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 3.003 W Design Power Budget: **Not Specified**


Power Budget Margin: N/A Junction Temperature: 30.7°C

54.3°C (28.7 W) Thermal Margin:

1.9°C/W Effective 9JA: Power supplied to off-chip devices: 0 W

<u>Launch Power Constraint Advisor</u> to find and fix invalid switching activity

Confidence level:

 

Q9.N-BIT COMPARATOR

VERILOG CODE:-

```
module comparator (
input wire [3:0] a,
input wire [3:0] b,
output reg equal,
output reg equal,
output reg lower,
output reg greater
);


always 0* begin
equal = 0;
lower = 1;
greater = 0;
end
else if (a==b) begin
equal = 1;
lower = 0;
greater = 0;
end
else begin
equal = 0;
lower = 0;
greater = 0;
end
else begin
equal = 0;
lower = 0;
greater = 1;
end
end
endmodule
```

TEST BENCH:-


\$finish;

end endmodule

```
module testcomp;
teg (100) a, b;
vire eq. M., gr;
vore eq. M., gr;
.equal(eq),
.lower(lw),
.greater(gr)
);
initial begin
a = 0;
repeat (16) begin
b = 0;
repeat (16) begin
sito;
Sdimplay ("TESTING &d and &d yields eq=&d lw=&d gr=&d", a, b, eq. lw, gr);
if (aw=b as eq!=1"b1 as gr!=1"b0 as lw!=1"b0) begin
sdimplay ("RECRIT");
Sfinish;
end
if (abb as eq!=1"b1 as gr!=1"b0 as lw!=1"b0) begin
Sdimplay ("GERCRIT");
Sfinish;
end
b = b + 1;
end
a = a + 1;
end
sdimplay ("PASSED!");
Sfinish;
```

 

SYNTHESIS REPORT:-

 

POWER REPORT:-

Summary


Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 1.009 W Design Power Budget: Not Specified Power Budget Margin: N/A Junction Temperature: 26.9°C

Thermal Margin: 58.1°C (30.7 W) Effective 9JA: 1.9°C/W

Power supplied to off-chip devices: 0 W Confidence level:
 
<u>Launch Power Constraint Advisor</u> to find and fix invalid switching activity



Q10. SERIAL IN SERIAL OUT SHIFT REGISTER


VERILOG CODE:-

```
module siso_design(input clk,b,output q);
wire w1,w2,w3;
d_ff dutl(.clk(clk),.d(b),.q(wl),.rst());
d_ff dut2(.clk(clk),.d(w1),.q(w2),.rst());
d_ff dut3(.clk(clk),.d(w2),.q(w3),.rst());
d_ff dut4(.clk(clk),.d(w3),.q(q),.rst());
endmodule
// d flip flop
module d_ff (
 input clk,
  input d,
 input rst,
 output reg q);
  always @(posedge clk)
  begin
   if (rst)
     q <= 1'b0;
   else
      q \le d;
```


endmodule

TEST BENCH:-
 
```
// testbench
module siso_tb();
reg clk,b;
wire q;
siso_design uut(.clk(clk),.b(b),.q(q));
j initial
begin
clk=1'b0;
forever #5clk=~clk;
end
initial
9 begin
$monitor("clk=%d,b=%d,q=%d",clk,b,q);
initial
9 begin
b=1;
 #10;
b=1;
 #10;
 b=1;
 #10;
 b=0;
 #50;
$finish;
end
endmodule
```



SYNTHESIS REPORT:-

 

POWER REPORT:-

Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.351 W
Design Power Budget: Not Specified


Power Budget Margin: N/A
Junction Temperature: 25.7°C

Thermal Margin: 59.3°C (31.3 W)

Effective 9JA: 1.9°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low

Launch Power Constraint Advisor to find and fix


invalid switching activity

 


Q11. SERIAL IN PARALLEL OUT SHIFT REGISTER

VERILOG CODE:-

TEST BENCH:-

 

SYNTHESIS REPORT:-

 

POWER REPORT:-

Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 1.079 W
Design Power Budget: Not Specified


Power Budget Margin: N/A
Junction Temperature: 27.0°C

Thermal Margin: 58.0°C (30.6 W)

Effective \$JA: 1.9°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low

<u>Launch Power Constraint Advisor</u> to find and fix

invalid switching activity

 

Q12. PARALLEL IN PARALLEL OUT REGISTER

VERILOG CODE:-

```
timescale lns / lps
module pipo_design(input clk,input [3:0]b,output[3:0]a);

d_ff dl(.clk(clk),.d(b[3]),.q(a[3]),.rst());
 d_ff d2(.clk(clk),.d(b[2]),.q(a[3]),.rst());
 d_ff d3(.clk(clk),.d(b[3]),.q(a[3]),.rst());

d_ff d4(.clk(clk),.d(b[3]),.q(a[3]),.rst());

endmodule


// d flip flop

module d_ff (
   input clk,  // clock input
   input clk,  // data input
   input rst,  // asynchronous reset input
   output reg q // output
);


sawys @(posedge clk ) begin
   if (rst) // asynchronous reset
   q <= 1*b0;
   else // normal operation
   q <= d;
   end

endmodule</pre>
```

 
```
// test bench
module pipo_tb();
 reg clk;
  reg [3:0]b;
  wire [3:0]a;
  pipo_design uut(.clk(clk),.b(b),.a(a));
initial
begin
 clk=0;
  forever #10clk=~clk;
) initial
begin
  #10;
  b=4'b1000;
  #10;
 b=4'b0101;
  #10;
  $display("clk=%d,b=%d,a=%d",clk,b,a);
  #100 $finish;
endmodule
```



SYNTHESIS REPORT:-

 


POWER REPORT:-

 

 
Q13. PARALLEL IN SERIAL OUT REGISTER VERILOG CODE:-



```
module Shiftregister_PISO_tb();
reg [3:0]Parallel_in
reg Clk, load;
wire Serial out;
piso_design dut(Clk,load,Parallel_in,Serial_out);
initial begin
Clk=1'b0;
forever #5 Clk=~Clk;
initial begin
load=0;b=4'b0101;
#20 load=1;
#20 load=1;
#10 load=0;
#10 load=0;
#100 $finish;
end
endmodule
```



SYNTHESIS REPORT:-

 

Finished Writing Synthesis Report : Time (s): cpu = 00:00:15 ; elapsed = 00:00:51 . Memory (MB): peak = 1015.211 ; gain = 0.000

POWER REPORT:-

Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: Design Power Budget: 0.173 W

Power Budget Margin:

Not Specified N/A

Junction Temperature:

25.3°C

Thermal Margin:

59.7°C (31.5 W)

Effective 9JA:


1.9°C/W

Power supplied to off-chip devices: 0 W

Confidence level:

Launch Power Constraint Advisor to find and fix


invalid switching activity

 

 Q14. BIDIRECTION SHIFT REGISTER

VERILOG CODE:-


```
module tb_sr;
  parameter MSB = 16;
   reg data;
  reg clk;
  reg en;
  reg dir;
   reg rstn;
  wire [MSB-1:0] out;
   shift_reg #(MSB) sr0 ( .d (data),
                            .clk (clk),
                            .en (en),
                            .dir (dir),
                            .rstn (rstn),
                            .out (out));
   always #10 clk = ~clk;
   initial begin
     clk <= 0;
     en <= 0;
     dir <= 0;
     rstn <= 0;
     data <= 'h1;
   end
   initial begin
     rstn <= 0;
      #20 rstn <= 1;
         en <= 1;
     repeat (7) @ (posedge clk)
        data <= ~data;
      #10 dir <= 1;
     repeat (7) @ (posedge clk)
        data <= ~data;
      repeat (7) @ (posedge clk);
     $finish;
   end
endmodule
```



SYNTHESIS REPORT:-



POWER REPORT:-

 


Q15. PRBS SEQUENCE GENERATOR

VERILOG CODE:-

```
module prbs (rand, clk, reset);
input clk, reset;
output rand;
wire rand;
reg [3:0] temp;
always @ (posedge reset) begin
temp <= 4'hf;
end
always @ (posedge clk) begin
if (-reset) begin
temp <= {temp[0]^temp[1],temp[3],temp[2],temp[1]};
end
end
assign rand = temp[0];
endmodule</pre>
```
 
```
module pbrs_tb;
reg clk, reset;
 wire rand;
 prbs pr (rand, clk, reset);
initial begin
forever begin
 clk <= 0;
 #5
 clk <= 1;
 #5
 clk <= 0;
end
end
initial begin
 reset = 1;
  #12
 reset = 0;
 #90
 reset = 1;
 #12
 reset = 0;
end endmodule
```




SYNTHESIS REPORT:-



POWER REPORT:-

Summary

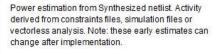

Total On-Chip Power:

0.1 W

Design Power Budget:

Not Specified N/A

Power Budget Margin: Junction Temperature:

25.2°C

Thermal Margin:

59.8°C (31.6 W)

Effective 9JA:

1.9°C/W


Confidence level:

Power supplied to off-chip devices: 0 W

Low

Launch Power Constraint Advisor to find and fix

invalid switching activity

 


Q16 & 17. 8-BIT ADDER/SUBTRACTOR

VERILOG CODE:-

```
module par_sub(a,b,cin,diff,bout);
 input [7:0] a;
  input [7:0] b;
  input cin;
  output reg [7:0] diff;
  output reg bout;
  reg [8:0] c;
 integer i;
always @ (a or b or cin)
begin
 c[0]=cin;
if (cin == 0) begin
for ( i=0; i<8 ; i=i+1)
) begin
 diff[i] = a[i]^b[i]^c[i];
 c[i+1] = (a[i] &b[i]) | (a[i] &c[i]) | (b[i] &c[i]);
) end
) end
else if (cin == 1) begin
for ( i=0; i<8 ; i=i+1)
) begin
 diff[i] = a[i]^(~ b[i])^c[i];
 c[i+1] = (a[i] & (\sim b[i])) | (a[i] & c[i]) | ((\sim b[i]) & c[i]);
) end
  bout=c[8];
) end
) endmodule
```

```
module par_sub_tb
reg [7:0] a;
reg [7:0] b;
reg cin;
wire [7:0] diff;
wire bout;
par_sub_uut (.a(a),.b(b),.cin(cin),.diff(diff),.bout(bout) );
initial begin
#10 a=8'b000000001;b=8'b00000001;cin=1'b0;
#10 a=8'b000000001;b=8'b00000001;cin=1'b1;
#10 a=8'b00000010;b=8'b00000011;cin=1'b0;
#10 a=8'b10000001;b=8'b10000001;cin=1'b0;
#10 a=8'b00011001;b=8'b00110001;cin=1'b0;
#10 a=8'b000000011;b=8'b00000011;cin=1'b1;
#10 a=8'b111111111;b=8'b00000001;cin=1'b0;
#10 a=8'b111111111;b=8'b00000000;cin=1'b1;
#10 a=8'b111111111;b=8'b111111111;cin=1'b0;
#10 $stop;
end
endmodule
```

 

SYNTHESIS REPORT:-


Start Writing Synthesis Report Report BlackBoxes: | |BlackBox name |Instances | Report Cell Usage: |Cell |Count | 11 ILUT2 | ILUT3 | 12 61 |3 |LUT5 | |IBUF | 15 IOBUF I 91 Report Instance Areas: |Instance |Module |Cells |

Finished Writing Synthesis Report : Time (s): cpu = 00:00:09 ; elapsed = 00:00:27 . Memory (MB): peak = 1017.555 ; gain = 0.000

POWER REPORT:-

Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis. Total On-Chip Power: 5.862 W Design Power Budget: Not Specified Power Budget Margin: N/A Junction Temperature: 36.0°C Thermal Margin: 49.0°C (25.8 W) 1.9°C/W Effective 9JA: Power supplied to off-chip devices: 0 W Confidence level: Launch Power Constraint Advisor to find and fix invalid switching activity

 


Q18. 4-BIT MULTIPLIER


VERILOG CODE:-

```
`timescale lns / lps
module multiplier_4_x_4(product,inpl,inp2);
   output [7:0]product;
    input [3:0]inpl;
   input [3:0]inp2;
   assign product[0]=(inpl[0]&inp2[0]);
   wire x1,x2,x3,x4,x5,x6,x7,x8,x9,x10,x11,x12,x13,x14,x15,x16,x17;
   HA HAl(product[1],xl,(inpl[1]&inp2[0]),(inpl[0]&inp2[1]));
    FA FA1(x2,x3,inp1[1]&inp2[1],(inp1[0]&inp2[2]),x1);
    FA FA2(x4,x5,(inpl[1]&inp2[2]),(inpl[0]&inp2[3]),x3);
   HA HA2(x6,x7,(inpl[1]&inp2[3]),x5);
   HA HA3(product[2],x15,x2,(inpl[2]&inp2[0]));
   FA FA5(x14,x16,x4,(inpl[2]&inp2[1]),x15);
   FA FA4(x13,x17,x6,(inp1[2]&inp2[2]),x16);
FA FA3(x9,x8,x7,(inpl[2]&inp2[3]),x17);
   HA HA4(product[3],x12,x14,(inpl[3]&inp2[0]));
    FA FA8(product[4],x11,x13,(inpl[3]&inp2[1]),x12);
   FA FA7(product[5],x10,x9,(inp1[3]&inp2[2]),x11);
    FA FA6(product[6],product[7],x8,(inpl[3]&inp2[3]),x10);
) endmodule
module HA(sout,cout,a,b);
   output sout, cout;
   input a,b;
    assign sout=a^b;
   assign cout=(a&b);
) endmodule
module HA(sout,cout,a,b);
   output sout, cout;
    input a,b;
    assign sout=a^b;
    assign cout=(a&b);
endmodule
module FA(sout,cout,a,b,cin);
    output sout, cout;
    input a,b,cin;
    assign sout=(a^b^cin);
    assign cout=((asb)|(ascin)|(bscin));
endmodule
```

```
module tb;
    reg [3:0]inpl;
    reg [3:0]inp2;
    wire [7:0]product;
    multiplier_4_x_4 uut(.inpl(inpl),.inp2(inp2),.product(product));
)
    initial
    begin
       inpl=10;
       inp2=12;
       #30 ;
       inpl=13;
       inp2=12;
       #30 ;
       inpl=10;
       inp2=22;
       #30 ;
       inpl=11;
       inp2=22;
       #30 ;
       inpl=12;
       inp2=15;
       #30 ;
       $finish;
     end
endmodule
```

 

SYNTHESIS REPORT:-

 

Finished Writing Synthesis Report : Time (s): cpu = 00:00:15 ; elapsed = 00:00:30 . Memory (MB): peak = 1014.992 ; gain = 0.000

POWER REPORT:-

Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power: 4.18 W

Design Power Budget: Not Specified

Power Budget Margin: N/A
Junction Temperature: 32.9°C


Thermal Margin: 52.1°C (27.5 W)

Effective 9JA: 1.9°C/W

Power supplied to off-chip devices: 0 W
Confidence level: Low

Launch Power Constraint Advisor to find and fix

invalid switching activity

 

Q19. FIXED POINT DIVISION


VERILOG CODE:-

```
initial reg_quotient = 0;
initial reg_working_dividend = 0;
initial reg_working_divisor = 0;
initial reg_count = 0;
assign \ o\_quotient\_out[N-2:0] \ = \ reg\_quotient[N-2:0];
assign o_quotient_out[N-1] = reg_sign;
assign o_complete = reg_done;
assign o_overflow = reg_overflow;
always @( posedge i_clk ) begin
    if( reg_done && i_start ) begin
        reg_done <= 1'b0;</pre>
        reg_count <= N+Q-1;</pre>
        reg_working_quotient <= 0;</pre>
         reg_working_dividend <= 0;</pre>
        reg_working_divisor <= 0;</pre>
        reg_overflow <= 1'b0;</pre>
         \label{eq:condition} {\tt reg\_working\_dividend[N+Q-2:Q]} \ <= \ i\_{\tt dividend[N-2:0]};
        reg\_working\_divisor[2*N+Q-3:N+Q-1] \ <= \ i\_divisor[N-2:0];
        reg_sign <= i_dividend[N-1] ^ i_divisor[N-1];</pre>
    else if(!reg_done) begin
        reg_working_divisor <= reg_working_divisor >> 1;
        reg_count <= reg_count - 1;</pre>
         // If the dividend is greater than the divisor
        if(reg_working_dividend >= reg_working_divisor) begin
             reg_working_quotient[reg_count] <= 1'bl;</pre>
             reg_working_dividend <= reg_working_dividend - reg_working_divisor;</pre>
```


```
//stop condition
if(reg_count == 0) begin
    reg_done <= l'bl;
    reg_quotient <= reg_working_quotient;
    if (reg_working_quotient[2*N+Q-3:N]>0)
        reg_overflow <= l'bl;
        end
    else
        reg_count <= reg_count - 1;
    end
end
endmodule</pre>
```

```
module Test_Div;
        // Inputs
       reg [31:0] i_dividend;
       reg [31:0] i_divisor;
       reg i_start;
       reg i_clk;
       // Outputs
       wire [31:0] o_quotient_out;
       wire o_complete;
       wire o_overflow;
        // Instantiate the Unit Under Test (UUT)
       qdiv uut (
           .i_dividend(i_dividend),
            .i_divisor(i_divisor),
           .i_start(i_start),
            .i_clk(i_clk),
            .o_quotient_out(o_quotient_out),
            .o_complete(o_complete),
            .o_overflow(o_overflow)
       reg [10:0] count;
       initial begin
            // Initialize Inputs
0000
            i dividend = 1;
           i_divisor = 1;
            i_start = 0;
            i_clk = 0;
            count <= 0;
```

```
// Wait 100 ns for global reset to finish
        #100;
        // Add stimulus here
        forever #2 i_clk = ~i_clk;
    end
        always @(posedge i_clk) begin
            if (count == 47) begin
                count <= 0;
                i_start <= 1'bl;</pre>
                end
            else begin
                count <= count + 1;</pre>
                i_start <= 1'b0;
            end
        always @(count) begin
            if (count == 47) begin
                if ( i_divisor > 32'hlfffffff ) begin
                     i_divisor <= 1;
                    i_dividend = (i_dividend << 1) + 3;</pre>
                    end
                    i_divisor = (i_divisor << 1) + 1;</pre>
                end
            end
    always @(posedge o_complete)
        $display ("%b,%b,%b, %b", i_dividend, i_divisor, o_quotient_out, o_overflow);
endmodule
```

 

SYNTHESIS REPORT:-

 

POWER REPORT:-




Q20. MASTER SLAVE JK FLIP FLOP


VERILOG CODE:-

```
module jk_flip_flop_master_slave(Q, Qn, C, J, K, RESETn);
     output Q;
     output Qn;
     input C;
     input J;
     input K;
     input RESETn;
     wire MQ;
     wire MQn;
     wire Cn;
     wire Jl;
     wire Kl;
     wire J2;
     wire K2:
     assign J2 = !RESETn ? 0 : J1;
     assign K2 = !RESETn ? 1 : K1;
     and(J1, J, Qn);
     and (K1, K, Q);
     not (Cn, C);
     sr_latch_gated master(MQ, MQn, C, J2, K2);
     sr_latch_gated slave(Q, Qn, Cn, MQ, MQn);
endmodule
module sr_latch_gated(Q, Qn, G, S, R);
    output Q;
    output Qn;
    input G;
    input S;
    input R;
    wire S1;
    wire R1;
    and (S1, G, S);
    and (R1, G, R);
    nor(Qn, S1, Q);
    nor(Q, R1, Qn);
endmodule
```

```
module JK_ff_tb;
 reg C, J, K, RESETn;
 wire Q;
 wire Qn;
 jk\_flip\_flop\_master\_slave \ jkflipflop(\ .C(C),\ .RESETn(RESETn),\ .J(J),\ .K(K),\ .Q(Q),\ .Qn(Qn)\ );
) initial begin
  $dumpfile("dump.vcd"); $dumpvars;
 $monitor(C, J, K, Q, Qn, RESETn);
 J = 1'b0;
 K = 1'b0;
 RESETn = 1;
 C=1;
 #10
 RESETn=0;
 J=1'b1;
 K=1'b0;
 #100
 RESETn=0;
 J=1'b0;
 K=1'b1;
 #100
 RESETn=0;
 J=1'b1;
 K=1'b1;
  #100
 RESETn=0;
  #100
  RESETn=0;
  J=1'b1;
  K=1'b1;
  #100
  RESETn=0;
  J=1'b0;
  K=1'b0;
  #100
  RESETn=1;
  J=1'b1;
  K=1'b0;
end
  always #25 C <= ~C;
endmodule
```

 

SYNTHESIS REPORT:-

 

POWER REPORT:-

Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power: 1.413 W
Design Power Budget: Not Specified


Power Budget Margin: N/A
Junction Temperature: 27.7°C

Thermal Margin: 57.3°C (30.2 W)

Effective 9JA: 1.9°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low

Launch Power Constraint Advisor to find and fix

invalid switching activity

 


Q21. POSITIVE EDGE DETECTOR

VERILOG CODE:-

```
module pos edge detect(clk,nrst,din,dout);
input clk;
input nrst;
input din;
output dout;
reg d_ff;
always @(posedge clk or negedge nrst)
begin
if(!nrst)
d_ff <= 1'b0;
else
d ff<=din;
assign dout=din&&(d_ff^din);
endmodule
module d_ff(D,C,a);
input D;
input C;
output a;
reg a;
always @(posedge C)
begin
 a <= D;
end
endmodule
```

```
module tb;
     reg nrst;
     reg clk;
     reg din;
     wire dout;
     pos_edge_det ped0 ( .nrst(nrst),
                          .clk(clk),
                         .din(din),.dout(dout));
     always #5 clk = ~clk;
     initial begin
         clk <= 0;
  nrst <= 0;
         #15 nrst<= 1;
          #20 nrst<= 0;
          #15 nrst<= 1;
         #10 nrst <= 0;
          #20 $finish;
     end
    initial begin
         $dumpvars;
       $dumpfile("dump.vcd");
end end
```

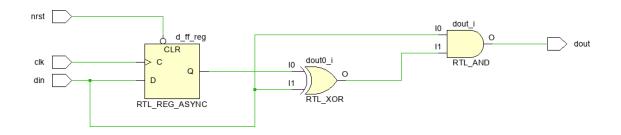

SYNTHESIS REPORT:-



POWER REPORT:-

Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power: 0.339 W

Design Power Budget: Not Specified

Power Budget Margin: N/A
Junction Temperature: 25.6°C


Thermal Margin: 59.4°C (31.3 W)

Effective &JA: 1.9°C/W

Power supplied to off-chip devices: 0 W
Confidence level: Low

Launch Power Constraint Advisor to find and fix

invalid switching activity

 

Q22. BCD ADDER


VERILOG CODE:-

```
module bcd_adder(a,b,carry_in,sum,carry);
      input [3:0] a,b;
     input carry_in;
     output [3:0] sum;
     output carry;
     reg [4:0] sum_temp;
     reg [3:0] sum;
     reg carry;
9
     always @(a,b,carry_in)
9
    begin
         sum_temp = a+b+carry_in;
         if(sum_temp > 9) begin
             sum_temp = sum_temp+6;
             carry = 1;
Ð
             sum = sum_temp[3:0]; end
         else begin
            carry = 0;
             sum = sum_temp[3:0];
Ė
         end
Ð
     end
) endmodule
```


TEST BENCH:-

```
module tb_bcdadder;
     reg [3:0] a;
     reg [3:0] b;
     reg carry_in;
     wire [3:0] sum;
     wire carry;
     bcd adder uut (
         .a(a),
         .b(b),
         .carry_in(carry_in),
         .sum(sum),
         .carry(carry)
     );
     initial begin
         a = 0; b = 0; carry_in = 0;
                                        #100;
         a = 6; b = 9; carry_in = 0;
                                        #100;
         a = 3; b = 3; carry_in = 1;
                                         #100;
                                        #100;
         a = 4; b = 5; carry_in = 0;
         a = 8; b = 2; carry_in = 0;
                                         #100;
         a = 9; b = 9; carry_in = 1;
                                         #100;
     end
) endmodule
```


RTL SCHEMATIC:-

 

SYNTHESIS REPORT:-

 

POWER REPORT:-

 

Q23. 4-BIT CARRY SELECT ADDER

VERILOG CODE:-


```
module carry select adder
            input [3:0] A,B,
              input cin,
              output [3:0] S,
              output cout
              );
  wire [3:0] temp0, temp1, carry0, carry1;
  fulladder fa00(A[0],B[0],1'b0,temp0[0],carry0[0]);
  fulladder fa01(A[1],B[1],carry0[0],temp0[1],carry0[1]);
  fulladder fa02(A[2],B[2],carry0[1],temp0[2],carry0[2]);
  fulladder fa03(A[3],B[3],carry0[2],temp0[3],carry0[3]);
  fulladder fal0(A[0],B[0],1'b1,templ[0],carry1[0]);
  fulladder fall(A[1],B[1],carryl[0],templ[1],carryl[1]);
  fulladder fal2(A[2],B[2],carryl[1],templ[2],carryl[2]);
  fulladder fal3(A[3],B[3],carryl[2],templ[3],carryl[3]);
  multiplexer2 mux_carry(carry0[3],carry1[3],cin,cout);
  multiplexer2 mux_sum0(temp0[0],temp1[0],cin,S[0]);
 multiplexer2 mux_suml(temp0[1],temp1[1],cin,S[1]);
  multiplexer2 mux_sum2(temp0[2],temp1[2],cin,S[2]);
  multiplexer2 mux_sum3(temp0[3],temp1[3],cin,S[3]);
) endmodule
```

```
module fulladder
        ( input a,b,cin,
            output sum, carry
 assign sum = a ^ b ^ cin;
 assign carry = (a & b) | (cin & b) | (a & cin);
) endmodule
module multiplexer2
        ( input i0,i1,sel,
            output reg bitout
            );
always@(i0,i1,sel)
begin
) if(sel == 0)
     bitout = i0;
 else
bitout = il;
end
) endmodule
```

TEST BENCH:-

```
) module tb_adder;
     reg [3:0] A;
     reg [3:0] B;
     reg cin;
     wire [3:0] S;
     wire cout;
     integer i,j,error;
     carry_select_adder uut (
         .A(A),
         .B(B),
         .cin(cin),
         .S(S),
         .cout (cout)
     );
initial begin
         A = 0;
         B = 0;
         error = 0;
         cin = 0;
      for(i=0;i<16;i=i+1) begin
             for(j=0;j<16;j=j+1) begin
                  A = i;
                  B = j;
                  #10;
                  if({cout,S} != (i+j))
```


RTL SCHEMATIC:-

 

SYNTHESIS REPORT:-

-	BlackBoxes		
	ckBox name		
+-+		+	+
Report.	Cell Usage	• •	
-	-++		
L	Cell Cou	int	
+	-+	+	
11	LUT3	2	
12	LUT5	4	
13	IBUF	91	
4	OBUF	5	
+	-+	+	
Denort	Instance A	lrese.	
-	-+		-++
İ	Instance		
	top		
+	-+	+	++

POWER REPORT:-

 

Q24. MOORE FSM 1010 SEQUENCE DETECTOR

VERILOG CODE:-


```
module morfsmolp(din, reset, clk, y);
input din;
input clk;
input reset;
output reg y;
reg [2:0] cst, nst;
parameter S0 = 3'b000,
         S1 = 3'b001,
          S2 = 3'b010,
          S3 = 3'b100,
           S4 = 3'b101;
always @(cst or din)
 begin
 case (cst)
   S0: if (din == 1'b1)
         begin
         nst = S1;
          y=1'b0;
          end
      else nst = cst;
   S1: if (din == 1'b0)
          begin
        nst = S2;
          y=1'b0;
          end
       else
          begin
          nst = cst;
          y=1'b0;
          end
   S2: if (din == 1'b1)
          begin
         nst = S3;
          y=1'b0;
          end
```

```
S3: if (din == 1'b0)
         begin
        nst = S4;
         y=1'b0;
          end
       else
          begin
          nst = S1;
         y=1'b0;
          end
S4: if (din == 1'b0)
         begin
         nst = S1;
         y=1'b1;
          end
          else
         begin
         nst = S3;
         y=1'b1;
          end
   default: nst = S0;
 endcase
end
always@(posedge clk)
begin
          if (reset)
          cst <= S0;
         else
           cst <= nst;
end
endmodule
```

TEST BENCH:-

```
module morfsmolp tb;
reg din,clk,reset;
wire y;
morfsmolp ml(din, reset, clk, y);
initial
begin
reset=0
              ;clk=0;din=0;
$monitor($time, , ,"c=%b",clk,,"y=%b",y,,"r=%b",reset,,"d=%b",din);
#10 din=1;
#10 din=0;
#10 din=1;
#10 din=0;
end
always
#5 clk=~clk;
initial
#100 $finish;
endmodule
```

RTL SCHEMATIC:-

 

SYNTHESIS REPORT:-

```
Start Writing Synthesis Report
Report BlackBoxes:
| |BlackBox name |Instances |
Report Cell Usage:
      |Cell |Count |
11
      |BUFG |
12
      ILUT2 |
       |LUT3 |
13
                  21
|4
      |LUT5 |
                  11
       |LUT6 |
15
                  11
       |FDSE |
18
      |LD |
                  11
19
       |IBUF |
                  3|
110
      IOBUF I
                11
Report Instance Areas:
      |Instance |Module |Cells |
11
    Itop
Finished Writing Synthesis Report : Time (s): cpu = 00:00:10 ; elapsed = 00:00:17 . Memory (MB): peak = 1017.680 ; gain = 0.000
```

POWER REPORT:-

Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

0.172 W

Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 25.3°C


Thermal Margin: 59.7°C (31.5 W)
Effective \$JA: 1.9°C/W

Power supplied to off-chip devices: 0 W
Confidence level: Low

Launch Power Constraint Advisor to find and fix

invalid switching activity

Total On-Chip Power:

 

Q25. N:1 MUX

VERILOG CODE:-

```
module mux_4_1(
    input [1:0] sel,
    input i0,il,i2,i3,
    output reg y);

always @(*) begin
    case(sel)
    2'h0: y = i0;
    2'h1: y = i1;
    2'h2: y = i2;
    2'h3: y = i3;
    default: $display("Invalid sel input");
    endcase
end
endmodule
```


TEST BENCH:-

```
module tb;
  reg [1:0] sel;
  reg i0,i1,i2,i3;
  wire y;

  mux_example mux(sel, i0, i1, i2, i3, y);

initial begin
  $monitor("sel = %b -> i3 = %0b, i2 = %0b ,i1 = %0b, i0 = %0b -> y = %0b", sel,i3,i2,i1,i0, y);
  {i3,i2,i1,i0} = 4'h5;
  repeat(6) begin
    sel = $random;
    #5;
  end
end
end
end
end
```

RTL SCHEMATIC:-

 

SYNTHESIS REPORT:-

```
Start Writing Synthesis Report
Report BlackBoxes:
| |BlackBox name |Instances |
Report Cell Usage:
     |Cell |Count |
     |LUT6 |
               1|
11
      |IBUF |
12
13
     |OBUF |
Report Instance Areas:
      |Instance |Module |Cells |
11
+----+
Finished Writing Synthesis Report : Time (s): cpu = 00:00:11 ; elapsed = 00:00:20 . Memory (MB): peak = 1020.262 ; gain = 0.000
```

POWER REPORT:-

Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power:

Design Power Budget:

Not Specified

N/A

Junction Temperature:

Thermal Margin:

Effective 9JA:

Power supplied to off-chip devices:

Confidence level:

Low

Launch Power Constraint Advisor to find and fix invalid switching activity

